

Analog IC Design

Lab 11 (Mini Project 02)

Fully-Differential Folded Cascode OTA

PART 1: gm/ID Design Charts

NMOS

 


Figure 1 NMOS GM/GDS VS GM/ID

 


Figure 2 NMOS ID/W VS GM/ID

 


Figure 3 NMOS GM/CGG VS GM/ID

 


Figure 4 NMOS VGS VS GM/ID

PMOS

 


Figure 5 PMOS GM/GDS VS GM/ID

 


Figure 6 PMOS I_D/W VS GM/I_D

 


Figure 7 PMOS GM/CGG VS GM/I_D

 


Figure 8 PMOS V_{GS} VS GM/I_D

For the input pair

$V_{ICM_LOW} = 0$, so the input pair we will be used is PMOS.
we will follow the Suggested Design Procedure

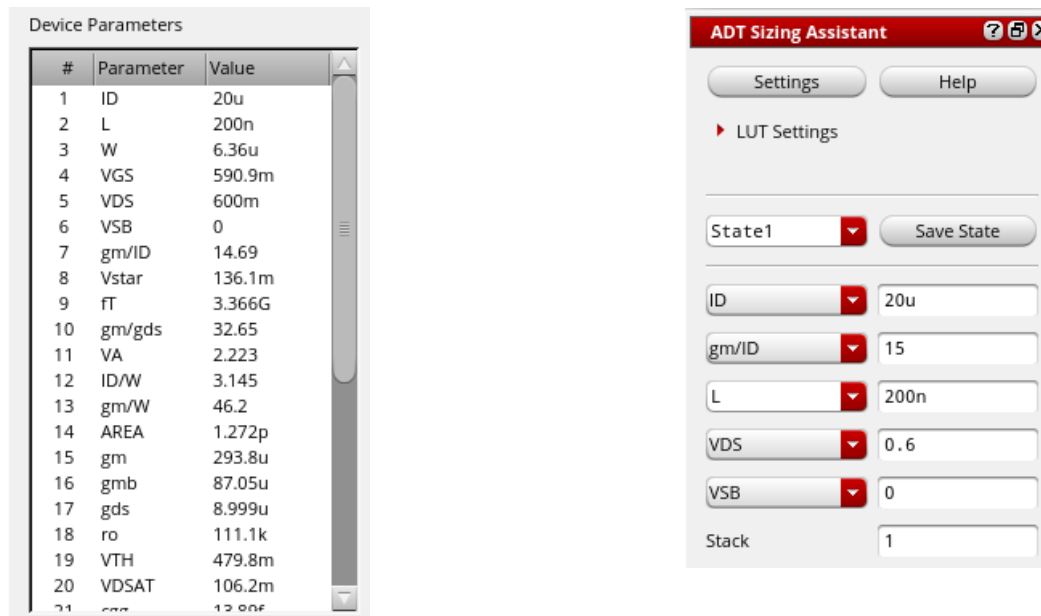


Figure 9 input pair

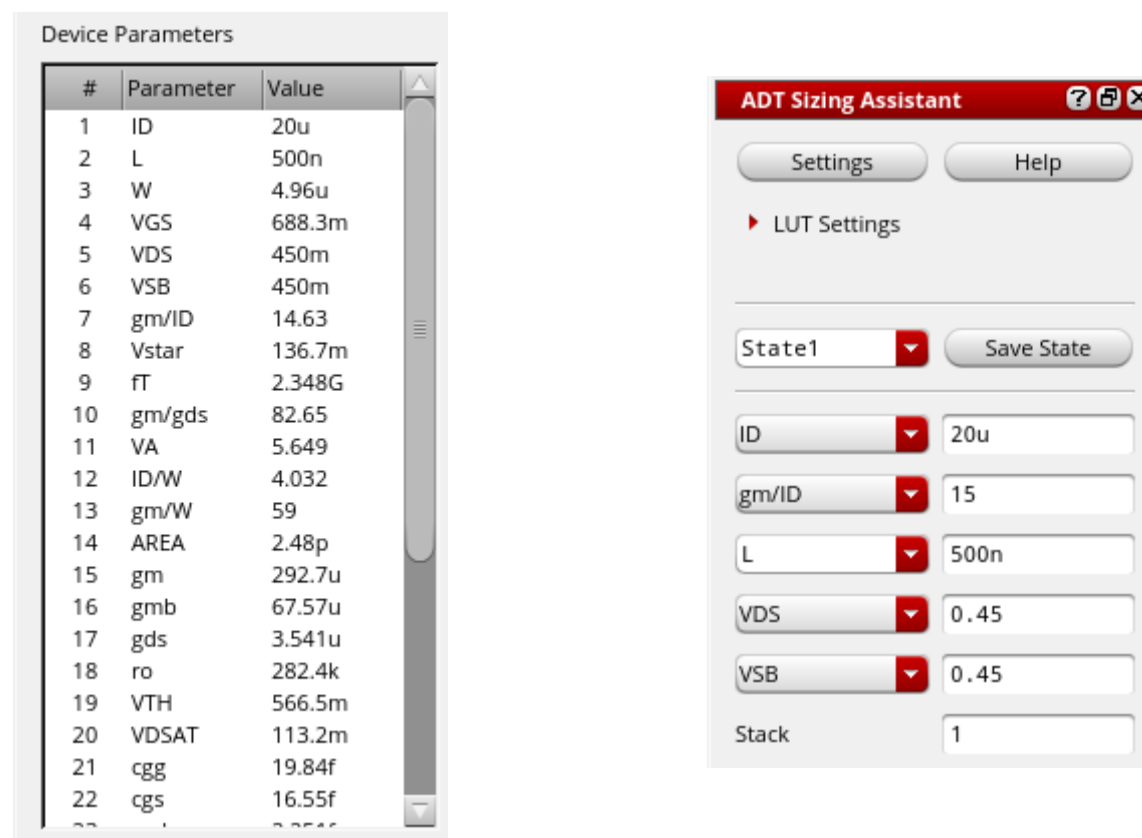


Figure 10 Nmos Cascode

#	Parameter	Value
1	ID	20u
2	L	500n
3	W	22.19u
4	VGS	674.4m
5	VDS	450m
6	VSB	450m
7	gm/ID	14.96
8	Vstar	133.7m
9	fT	507.3M
10	gm/gds	84.11
11	VA	5.622
12	ID/W	901.3m
13	gm/W	13.48
14	AREA	11.1p
15	gm	299.2u
16	gmb	78u
17	gds	3.557u
18	ro	281.1k
19	VTH	562.1m
20	VDSAT	110.2m
21	cgg	93.87f

ADT Sizing Assistant

Settings

Help

LUT Settings

State1

Save State

ID

20u

gm/ID

15

L

500n

VDS

0.45

VSB

0.45

Stack

1

Figure 11 Pmos Cascode

#	Parameter	Value
1	ID	20u
2	L	1u
3	W	4.29u
4	VGS	616.1m
5	VDS	450m
6	VSB	0
7	gm/ID	9.851
8	Vstar	203m
9	fT	961.2M
10	gm/gds	99.47
11	VA	10.1
12	ID/W	4.662
13	gm/W	45.93
14	AREA	4.29p
15	gm	197u
16	gmb	53.72u
17	gds	1.981u
18	ro	504.9k
19	VTH	406.2m
20	VDSAT	157.9m

ADT Sizing Assistant

Settings

Help

LUT Settings

State1

Save State

ID

20u

gm/ID

10

L

1u

VDS

0.45

VSB


0

Stack

1

Figure 12 Nmos current source

#	Parameter	Value
1	ID	20u
2	L	1u
3	W	17.47u
4	VGS	610.4m
5	VDS	450m
6	VSb	0
7	gm/ID	9.857
8	Vstar	202.9m
9	rT	234.7M
10	gm/gds	108.4
11	VA	11
12	ID/W	1.145
13	gm/W	11.28
14	AREA	17.47p
15	gm	197.1u
16	gmb	61.17u
17	gds	1.818u
18	ro	550.1k
19	VTH	409.6m
20	VDSAT	161.5m
21	gss	122.7f

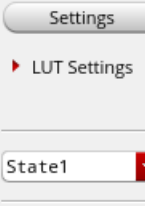

ADT Sizing Assistant

Settings Help

▶ LUT Settings

State1 Save State

ID 20u

gm/ID 10

L 1u

VDS 0.45

VSB 0

Stack 1

Figure 13 Pmos current source

$$VCASCN \approx VGSN + V^* \approx 688m + 203m = 791m$$

$$VCASCP \approx VDD - |VGSP| - V^* \approx 1.8 - 674m - 203m = 923m$$

PART 3: Open-Loop OTA Simulation (Behavioural CMFB)

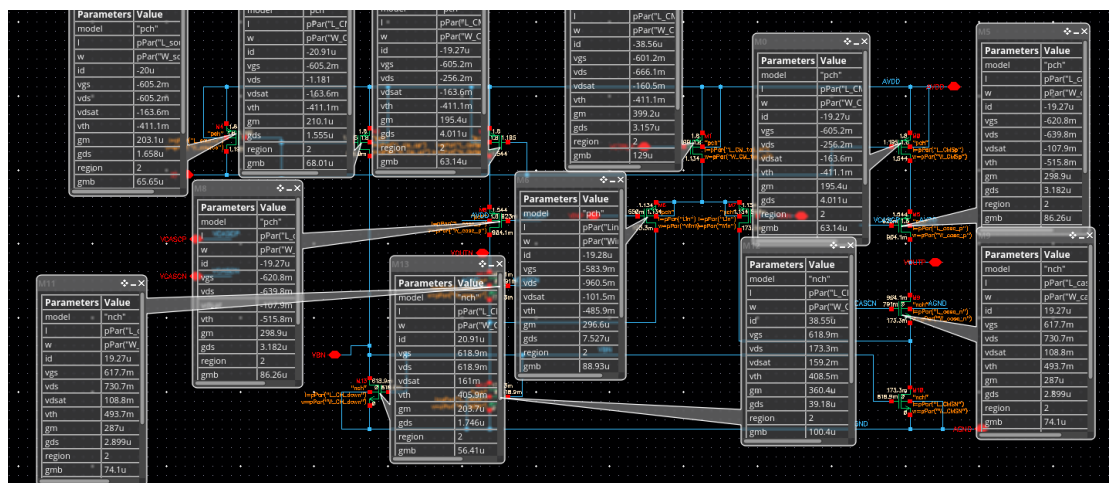


Figure 14 OP parameters

What is the CM level at the OTA output?

$$V_{OCM} = 904.1 \text{ m}$$

VDC("VOCM")	904.1m
-------------	--------

What are the differential input and output voltages of the error amplifier? What is the relation between them?

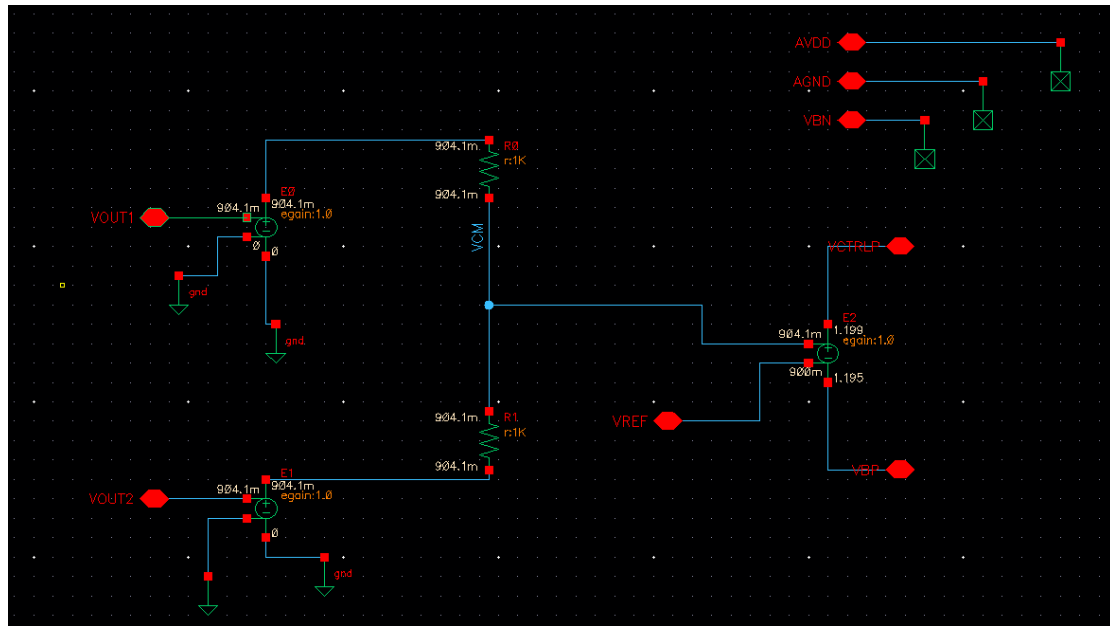


Figure 15 error amplifier

$$VIN_{diff} = 904.1m - 900m = 0.4 \text{ mV}$$

$$Vout_{diff} = 1.99 - 1.195 = 0.4 \text{ mV}$$

$$\frac{Vout_{diff}}{VIN_{diff}} = 1, \text{ as it work as a buffer}$$

2) Diff small signal ccs:

- Plot diff gain (magnitude in dB and phase) vs frequency.

 


Figure 16 diff gain (magnitude in dB) vs frequency

 


Figure 17 diff gain (phase) vs frequency

- Calculate circuit parameters (DC gain, BW, GBW, UGF, and PM).

Ao	expr	ymin(mag(VF("/VODIFF")))	725.7
Ao_dB	expr	dB20(ymin(mag(VF("/VODIFF"))))	57.22
BW	expr	bandwidth(VF("/VODIFF") 3 "low")	55.59K
UGF	expr	unityGainFreq(VF("/VODIFF"))	40.41M
GBW	expr	gainBwProd(VF("/VODIFF"))	40.44M
	expr	phaseMargin(VF("/VODIFF"))	88.12

Figure 18 circuit parameters

- Compare simulation results with hand calculations in a table (use SS parameters from OP simulation in your hand analysis).

$$A_o = G_m * R_{out}$$

$$G_m = g_{m_{in}} = 296.6 \mu S$$

$$R_{out} = RLFD_{cascN} || RLFD_{cascP}$$

$$R_{out} = \frac{\left(1 + \frac{(g_{m_{cascN}} + g_{mb_{cascN}})}{g_{ds_{folded}} + g_{ds_{input}}}\right)}{g_{ds_{cascN}}} // \frac{\left(1 + \frac{(g_{m_{cascP}} + g_{mb_{cascP}})}{g_{ds_{C-mirrorP}}}\right)}{g_{ds_{cascP}}}$$

$$= \frac{1 + \frac{(300\mu + 86\mu)}{4\mu}}{3.2\mu} // \frac{1 + \frac{(287\mu + 74\mu)}{39\mu}}{2.9\mu} = 30.5M // 3.54M \approx 3.17M\Omega$$

$$A_{vd} = 296.6 \mu \times 3.17M = 940V/V \approx 59.46dB$$

To calculate the bandwidth, we can notice that the load capacitance is much larger than the parasitic capacitances, hence we can calculate BW as follows:

$$BW \approx \frac{1}{2\pi R_{out} \times CL} = \frac{1}{2\pi \times 3.17M \times 1p} \approx 50.2kHz$$

$$GBW = A_{vd} \times BW = 940 \times 50.2k \approx 47MHz$$

$$f_u \approx GBW \approx 497MHz$$

$$PM = 90 - \tan^{-1} \left(\frac{GBW}{\omega_{p2}} \right)$$

 


Figure 19 zeros & poles

$$PM = 90 - \tan^{-1} \left(\frac{47M}{479.7M} \right) \approx 84.39 \text{ deg}$$

	Simulation	Hand analysis
DC_diff_gain	57.22dB	59.46dB
BW	55.6kHz	50.2kHz
GBW	40.4MHz	47MHz
UGF	40.44MHz	47MHz
PM	88.12	84.39 deg

PART 4: Open-Loop OTA Simulation (Actual CMFB)

we will follow the Suggested Design Procedure

#	Parameter	Value
1	ID	10u
2	L	1u
3	W	23.1u
4	VGS	527.5m
5	VDS	900m
6	VSb	0
7	gm/ID	14.89
8	Vstar	134.4m
9	fT	136.7M
10	gm/gds	157.8
11	VA	10.6
12	ID/W	432.9m
13	gm/W	6.444
14	AREA	23.1p
15	gm	148.9u
16	gmb	45.78u
17	gds	943.4n
18	ro	1.06M
19	VTH	409.6m
20	VDSAT	103.9m

ADT Sizing Assistant
?
⏏

Settings
Help

▶ LUT Settings

State1
Save State

ID
10u

gm/ID
15

L
1u

VDS
0.9

VSb
0

Figure 20 PMOS pair

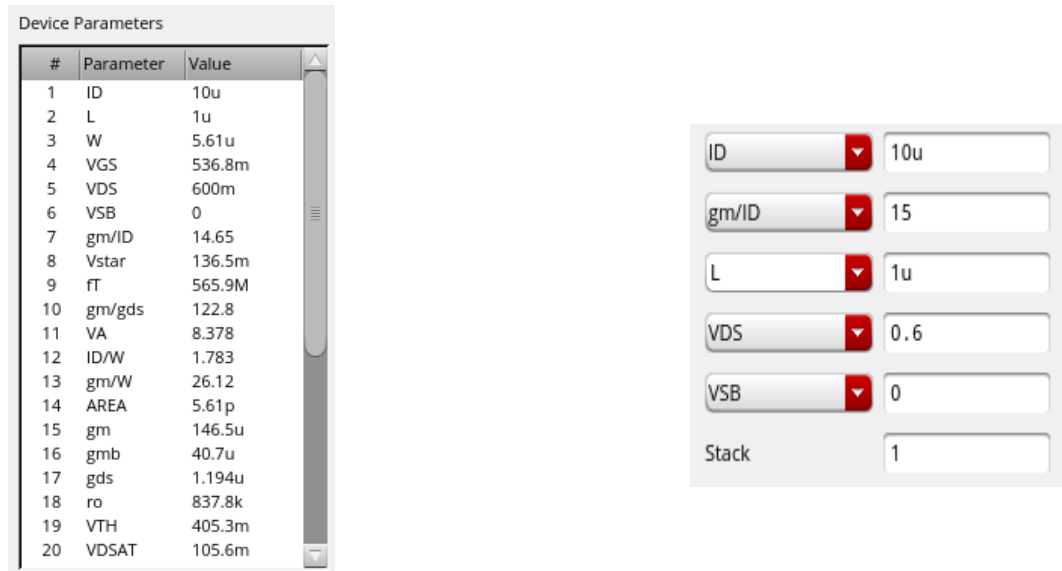


Figure 21 NMOS pair

$$V_{out_max} = V_{DD} - V_{GSP} - V^* = 1.8 - 620\text{ m} - 134\text{ m} = 1.046$$

$$V_{out_min} = 2 * V^* = 268\text{ m}$$

$$V_{out_cm_avg} = \frac{(V_{out_max} + V_{out_min})}{2} = 0.657\text{m}$$

$$V_{REF} = V_{out_cm_avg} + V_{GSP} = 0.657\text{m} + 527.5\text{m} = 1.185$$

1) Schematic of the OTA and CMFB circuit with DC node voltages and transistors OP parameters (id, vgs, vds, vdsat, vth, gm, gds, region) clearly annotated.

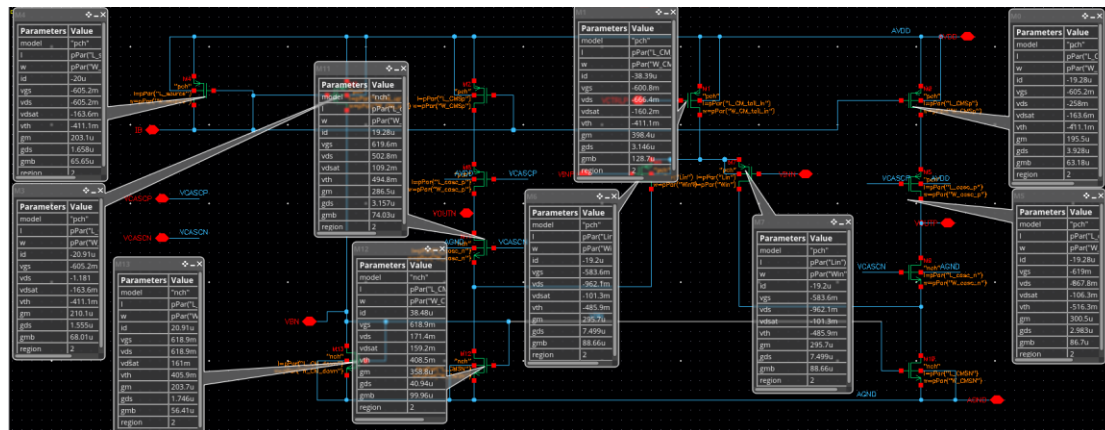


Figure 22 transistors OP parameters

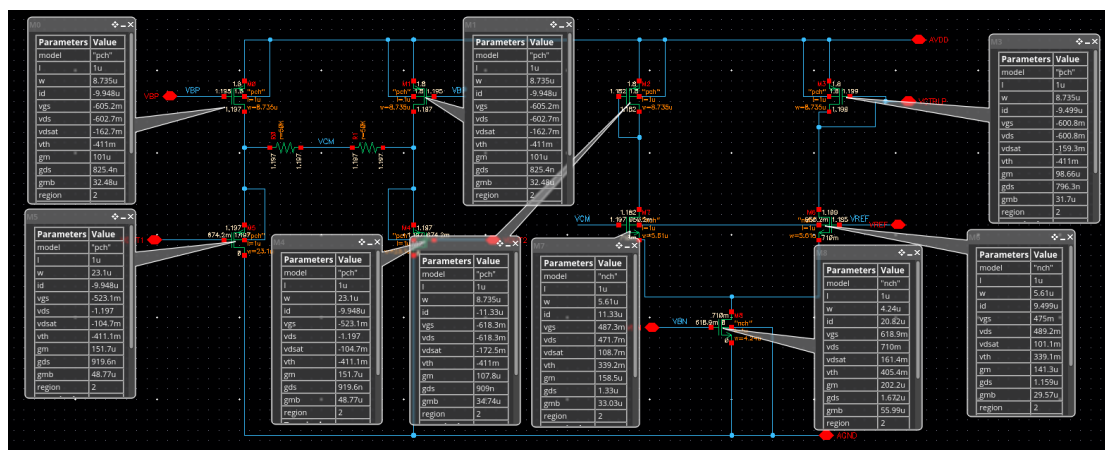


Figure 23 transistors OP parameters

What is the CM level at the OTA output? Why?

VDC("VOCM") 674.2m

As we designed the actual CMFB network to obtain a common mode of nearly 0.657 mV to maximize the output swing.

What are the differential input and output voltages of the error amplifier? What is the relation between them?

$$V_{indiff} = 1.197 - 1.185 = 12mV$$

$$V_{outdiff} = VGS_5 - VGS_2 = 1.199 - 1.182 = 17mV$$

$$\frac{V_{outdiff}}{V_{indiff}} = \frac{gm_{in} + gmb_{in}}{gm_{CM}} \approx 1.417$$

the gain of the error amplifier = $\frac{V_{outdiff}}{V_{indiff}}$

2) Diff small signal ccs:

- Plot diff gain (magnitude in dB and phase) vs frequency.

 


Figure 24 diff gain (magnitude) vs frequency

 


Figure 25 diff gain (phase) vs frequency

- Calculate circuit parameters (DC gain, BW, GBW, UGF, and PM).

Ao	expr	ymax(mag(VF("VODIFF")))	651
Ao_dB	expr	dB20(ymax(mag(VF("VODIFF"))))	56.27
BW	expr	bandwidth(VF("VODIFF") 3 "low")	59.47K
UGF	expr	unityGainFreq(VF("VODIFF"))	38.9M
GBW	expr	gainBwProd(VF("VODIFF"))	38.81M
	expr	phaseMargin(VF("VODIFF"))	88.15

Figure 26 circuit parameters

PART 5: Closed Loop Simulation (AC and STB Analysis)

In part 2 we started with an initial point by assuming values for L and gm/ID for the folded cascode, in this part we change these values but keeping the same ratios for the currents and W and L based on designer's experience and trade-offs.

CL	1p
IB	-20u
L_casc_n	0.9u
L_casc_p	0.9u
L_CM_d...	3u
L_CM_ta...	1.2u
L_CM_up	1.2u
L_CM_SN	3u
L_CM_Sp	1.2u
L_source	1.2u
Lin	350n
VCASCN	950m
VCASCP	850m
VICM	0.55
VICMac	0
VID	0
VIDac	1
VREF	1.185
W_casc_n	4.96u
W_casc_p	22.19u
W_CM_...	4.29u
W_CM_t...	17.47u
W_CM_up	17.47u
W_CM_SN	4.29u
W_CM_Sp	17.47u
W_source	17.47u
Win	25u
L2_Nin	1u
L2_Pin	1u
L2_VCTR...	1u
L2_VP	1u
W2_Nin	5.61u
W2_Pin	23.1u
W2_tail	4.24u
W2_VCT...	8.735u
W2_VP	8.735u
L2_tail	1u

Figure 27 final Tuning Results

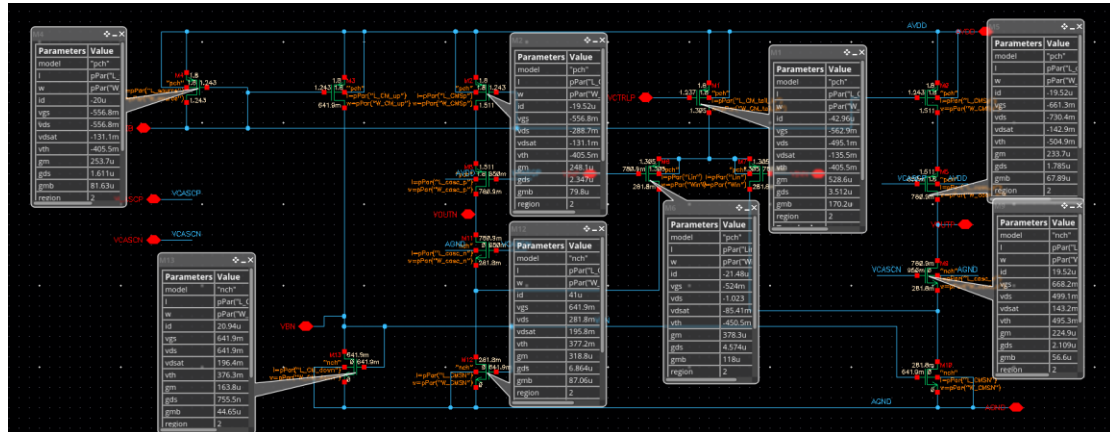


Figure 28 OTA

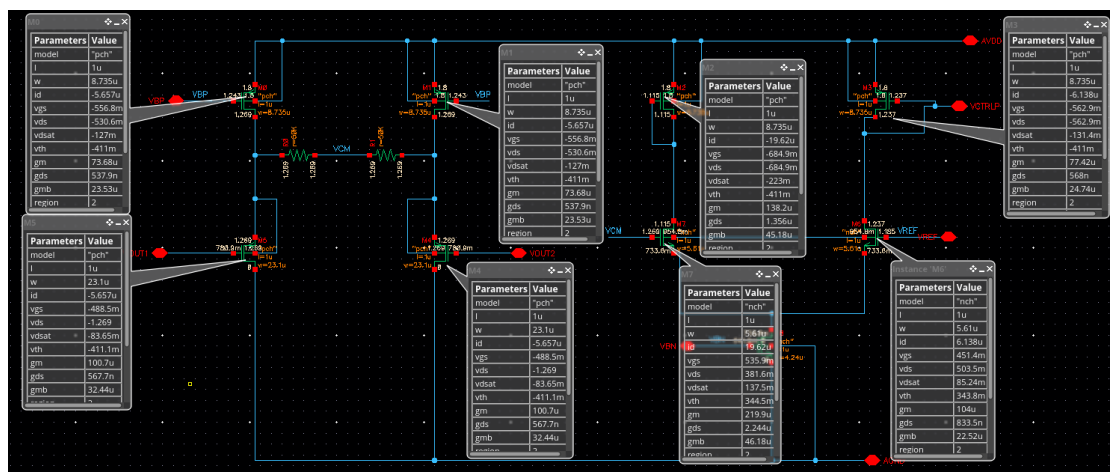


Figure 29 CMFB circuit

the CM level at the OTA output = 781m

VOCM	expr	VDC("VOCM")	780.9m
------	------	-------------	--------

As we designed the actual CMFB network to obtain a common mode of nearly 0.657 mV to maximize the output swing. But because of the limited gain the CMFB network will not be so accurate.

the CM level at the OTA input =781m

VICM	expr	((VDC("VFBP") + VDC("VFBN")) / 2)	780.9m
------	------	-----------------------------------	--------

It is same as the CM level at the OTA output because the feedback connection is a large resistor which make the input and output voltage equal.

2) Differential closed-loop response:

- Plot VODIFF vs frequency

 


Figure 30 VODIFF vs frequency

- Use Measures or cursors to calculate circuit parameters (DC gain, CL BW, CL GBW)

 


Figure 31 circuit parameters

Ao	expr	ymax(mag(VF("VODIFF")))	1.998	✓
Ao_dB	expr	dB20(ymax(mag(VF("VODIFF"))))	6.014	✓
BW	expr	bandwidth(VF("VODIFF") 3 "low")	12.17M	✓
UGF	expr	unityGainFreq(VF("VODIFF"))	21.9M	✓
GBW	expr	gainBwProd(VF("VODIFF"))	24.08M	✓
	expr	phaseMargin(VF("VODIFF"))	94.63	✓

Figure 32 Measures

3) Differential and CMFB loops stability (STB analysis):

 


Figure 33 DIFF LG in dB & phase vs frequency overlaid

 


Figure 34 CM LG in dB & phase vs frequency overlaid

• Compare GBW and PM of diff and CM loops. Comment.

LG_dB	expr	dB20(ymax(mag(getData("loopGain" ?result "stb"))))	62.08
GBW_LG	expr	gainBwProd(mag(getData("loopGain" ?result "stb")))	10.88M
BW_LG	expr	bandwidth(mag(getData("loopGain" ?result "stb"))) 3 "low"	8.536K
	expr	unityGainFreq(getData("loopGain" ?result "stb"))	11.11M

Figure 35 DIFF Mode

phaseMargin(deg)=88.529821

LG_dB	expr	dB20(ymax(mag(getData("loopGain" ?result "stb"))))	69.91
GBW_LG	expr	gainBwProd(mag(getData("loopGain" ?result "stb")))	17.99M
BW_LG	expr	bandwidth(mag(getData("loopGain" ?result "stb"))) 3 "low"	5.734K
	expr	unityGainFreq(getData("loopGain" ?result "stb"))	20.56M

Figure 36 CM

phaseMargin(deg)=72.366094

	DIFF	CM
GBW	10.88M	20.56M
PM	91 deg	72 deg

We notice that CM GBW is higher than DIFF GBW which means faster effect.

• Compare DC LG and GBW of the diff loop with those obtained from open-loop simulation.

LG_dB	expr	dB20(ymax(mag(getData("loopGain" ?result "stb"))))	73.24
GBW_LG	expr	gainBwProd(mag(getData("loopGain" ?result "stb")))	39.78M
BW_LG	expr	bandwidth(mag(getData("loopGain" ?result "stb")) 3 "low")	8.643K
	expr	unityGainFreq(getData("loopGain" ?result "stb"))	37.24M

Figure 37 open-loop simulation

	diff loop	open-loop
GBW	10.88M	39.78M
DC_LG	62 dB	73.24 dB

Comment

$$\text{open} - \text{loop DC} + 20 \log\left(\frac{1}{3}\right) = 73 - 9.5 = 63.5 \text{ dB} \approx \text{diff loop}$$

$$\text{open} - \text{loop GBW} * \frac{1}{3} = 13 \approx \text{diff GBW}$$

The error Because the feedback factor $\beta \approx \frac{1}{3}$ but not exactly equal it as we didn't add the parasitic capacitance in our calculations or the the loading effect of the feedback.

PART 6: Closed Loop Simulation (Transient Analysis)

1) Differential and CMFB loops stability (transient analysis):

 


Figure 38 transient signals DIFF

The differential outputs have no ringing because its phase margin is 91 which means that the system is overdamped that is meaning that it is slow but also it is a stable system so it has an adequate PM and no ringing.

The CM output has a small ringing as its phase margin is 72 which means that the system is underdamped so it hasn't an adequate PM and it should be higher but it's a stable system.

 


Figure 39 transient signals CM

 


Figure 40 transient signals CM overloaded

The CM output has a small ringing as its phase margin is 72 which means that the system is underdamped so it hasn't an adequate PM and it should be higher but it's a stable system.

We mentioned above that the diff mode has adequate PM, but Common mode hasn't, so it is appeared that in the differential output there is no ringing as the signals have the same values and sign.

The system is stable, and the effect of the ringing isn't considered as it is in the Common mode, but there is no ringing in the Diff mode.

2) Output swing:

- Plot the transient signals at VINP, VINN, VOUTP, VOUTN, and VOCM overlaid in the same figure.

 


Figure 41 transient signals

- Plot the transient signals at VIDIFF and VODIFF overlaid in the same figure.

 


Figure 42 VIDIFF and VODIFF overlaid.

- Calculate the diff input and output peak-to-peak swings and the closed loop gain.

PP_VIDIFF	expr	peakToPeak(VT("/net3"))	300m
PP_VODIFF	expr	peakToPeak(VT("/VODIFF"))	599.2m
Ao_CL	expr	(peakToPeak(VT("/VODIFF")) / peakToPeak(VT("/net3")))	1.997

output peak-to-peak swings = 300m

input peak-to-peak swings =600m

closed loop gain = 2