

Analog IC Design – Cadence Tools & SA

Lab 05

Simple vs Wide Swing (Low Compliance) Cascode Current Mirror

Part 1: Exploring Sizing Trade-offs Using SA

Answer the following:

2) The % Change in current translates to a spec on the $\lambda = 1/V_A$ of the device. How much is the required λ ?

$$I_D = \beta V_{OV}^2 (1 + \lambda V_{DS}) = \beta V_{OV}^2 (1 + \lambda V_{OUT})$$

$$\Delta I_D = \beta V_{OV}^2 \lambda \Delta V_{OUT}$$

$$\frac{\Delta I_D}{I_D} = \frac{\lambda \Delta V_{OUT}}{1 + \lambda V_{OUT}} \approx \lambda \Delta V_{OUT} \rightarrow \lambda = 0.1$$

3) Sinking current means which device type? NMOS or PMOS?

The device type is NMOS.

4) The higher the gm/I_D (the lower the V^*) the higher the headroom (the available swing), but the larger the area. Examine this trade-off using SA as shown below. Report L and W vs V_{star} .

 


Figure 1 L VS Vstar

 


Figure 2 W VS Vstar

6)

 


Figure 3 a bias point (Vstar) that gives idmis < 5%

$idmis = 2\%$, $V^* = 126.2113mV$

$W = 10.3u$

$L = 1.5u$

7) Can we do the previous design trade-offs exploration sweeps using a standard SPICE simulator, i.e., sweep Vstar at a constant λ ? Why?

NO, as We cannot guarantee the stability of all parameters in the emulator, and if we change one of the parameters to suit the design, another may change in a way that does not suit it. The goal is for all parameters to be in the allowed range with all changes λ is a parameter of the state on which the transistor is located, so this can be applied to it.

Part 2: Current Mirror Simulation

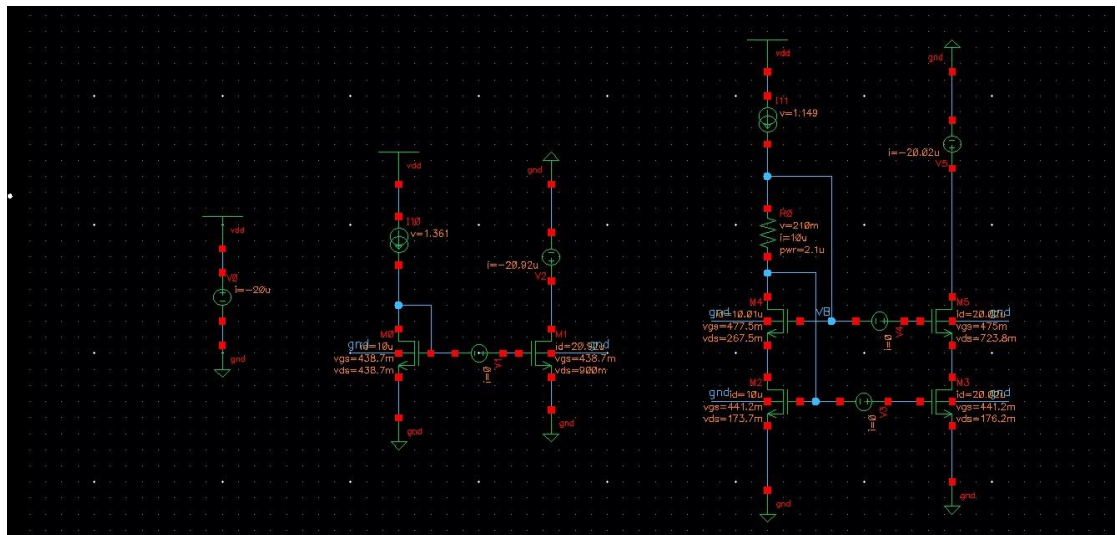


Figure 4 schematic

1. Design and OP (Operating Point) Analysis

1) calculate a rough value for $R_B = \frac{V_{DS3}}{I_B} = 17.6 \text{ K}\Omega$

2)

 


Figure 5 V_{DS3} vs R_B

Is the selected R_B value larger or smaller than the rough analytical value? Why?

Larger, Because we ignored the body effect in the analytical calculation which causes V_{th} to be changed from the simulation value so V_{GS} will be effected by V_{th} and R_B will be larger than the analytical value.

3)

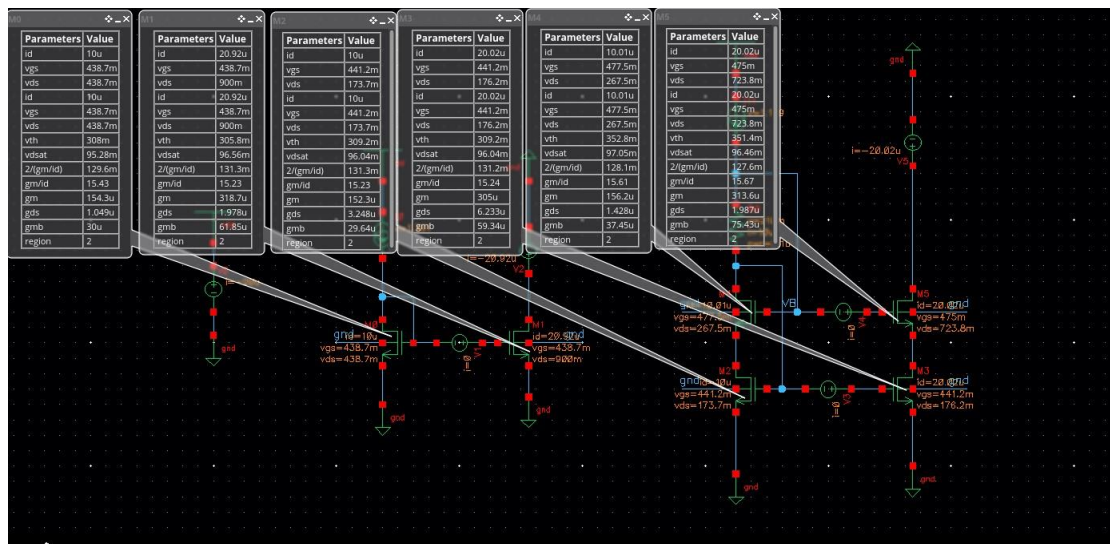


Figure 6 the OP point

4) Do all transistors operate in saturation?

YES.

2. DC Sweep (I_{out} vs V_{OUT})

 


Figure 7 I_{out} vs V_{OUT}

o Comment on the difference between the two circuits.

the first circuit is the simple CS Which hasn't the same V_{ds} for the two transistor M0 ,M1 that make little variation in the output current and the curve in the saturation region will be proportional to V_{out} , Unlike the wide swing one Which has the same V_{ds} for the two transistor M2 ,M3 that make the slope of the curve constant in the saturation region.

o From the plot, find an estimate for the compliance voltage of each current mirror.

 


Figure 8 the compliance voltage of I_1

the compliance voltage for simple CS = 91.2m


 


Figure 9 the compliance voltage of I2

the compliance voltage for wide swing (cascode) CS = 209.6m

 o I_{out} of the simple CM is exactly equal to $I_B \cdot 2$ at a specific value of V_{OUT} . Why?



for simple CS = 458.7m

for wide swing (cascode) CS = 461.3m

Because the current mirror act as a perfect current mirror when V_{ds} of the two transistors of the mirror become the same.

- 2) For the simple current mirror, calculate the percent change in I_{out} when V_{OUT} changes from 0.5V to 1.5V (i.e., 1V change). Compare the result to the value expected from Part 1.

 


Figure 10 V_{OUT} changes from 0.5V to 1.5V

the percent change = 10%

The Change in Current (ΔI_D) for Change in the output Voltage $\Delta V_{out} = 1V < 10\%$ from part 1.

- 3) Report the percent of error in I_{out} vs V_{OUT} (ideal I_{out} should be $I_B \cdot 2$) for the two CMs in the current mirror operating region ($V_{OUT} \approx V^*$ to V_{DD}) overlaid in the same plot.

 


Figure 11 the percent of error in I_{out} vs V_{OUT}

o Comment on the difference between the two circuits.

The wide-swing current mirror has no affects by V_{ds} compared with the simple CS current mirror, so it has better efficiency than the simple current mirror so the error in the wide-swing is less than the simple current mirror, and as the wide-swing current mirror act as cascode, so it has more R_{out} , and error almost equal zero, as M4&M5 make V_{DS} on M2&M3 equal.

- 4) Report R_{out} vs V_{OUT} (take the inverse of the derivative of I_{out} plot) for the two CMs in the current mirror operating region ($V_{OUT} \approx V^*$ to V_{DD}) overlaid in the same plot. Use log scale on the y-axis. Add a cursor at $V_{OUT} = V_{DD}/2$.

 


Figure 12 Figure 12 R_{out} VS V_{out}

o Comment on the difference between the two circuits.

R_{out} of wide-swing current mirror is more than that of simple current mirror, as output of wide swing current mirror act as a cascade amplifier that has high R_{out} compared with the simple current mirror.

o Does R_{out} change with V_{OUT} ? Why?

Yes, as R_{out} proportional with V_{ds} on the transistor, for simple CS V_{ds} is the same V_{out} and it directly effect on R_{out} , but for cascode CS there are two transistors (M3,M5) ,M3 has constant V_{ds} , but M5 effected by V_{out} and that what make R_{out} in the second circuit changes.

- 5) Analytically calculate Rout of both circuits at V results in a table.

Hand analysis:

$$R_{out_{simple}} = r_{o1} = \frac{1}{g_{ds1}} = \frac{1}{1.978\mu} = 505.6 \text{ K}\Omega$$

$$R_{out_{wide}} = \frac{(g_{m5} + g_{mbs})}{g_{ds5} * g_{ds3}} = \frac{(313.6\mu + 75.43\mu)}{1.987\mu * 6.233\mu} = 31.41 \text{ M}\Omega$$

	Simulator	Analytical
Simple Current Mirror	488.556 KΩ	506.5KΩ
wide-swing Current Mirror	31.8154 MΩ	31.41MΩ

3. Mismatch

- 1) Set VMIS1 = 5m/sqrt(W*L) and VMIS2 = 0.

This models the standard deviation of the mismatch in V_{TH} for the current mirror devices. Run OP simulation. Find the percent change in I_{out} .

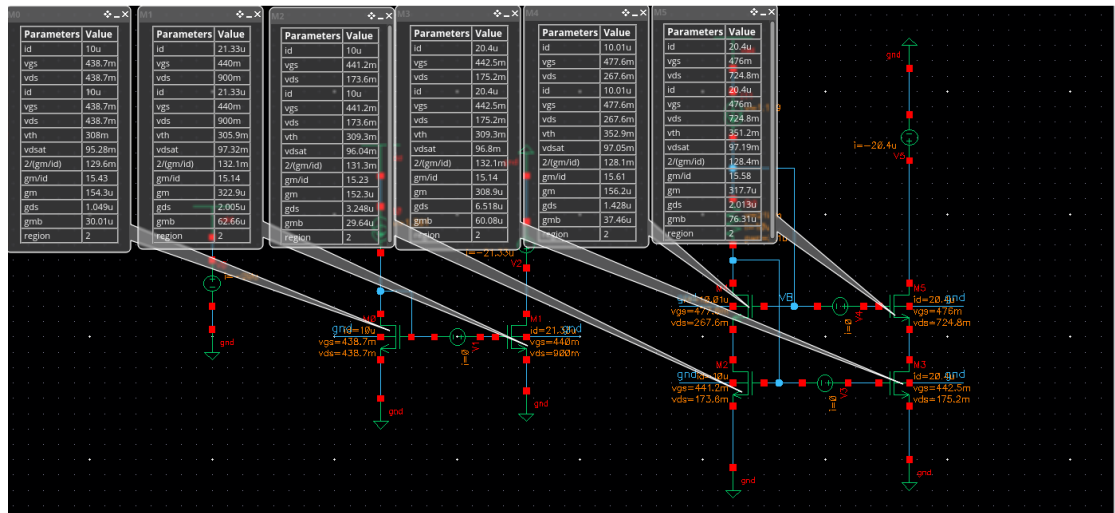


Figure 13 schematic with mismatch in V_{TH}

For simple CS : the percent change in $I_{out} = \frac{21.33u - 20.92u}{20.92u} = 1.96\%$

For Cascoded CS : the percent change in $I_{out} = \frac{20u - 20.4u}{20u} = 2\%$

- 2) Analytically calculate the percent change in I_{out} and compare it to the simulation result.

$$\Delta I = G_M \Delta V = g_m \Delta V = \frac{2 I_D * \Delta V}{V^*}$$

$$\frac{\Delta I}{I} = \frac{2 \Delta V}{V^*} = \frac{2 * V_{MIS}}{V^*} * 100 = 2\%$$

	Simulator	Analytical
Error %	1.96% , 2%	2%

- 3) Set VMIS1 = 0 and VMIS2 = 5m/sqrt(W*L). This models the standard deviation of the mismatch in V_{TH} for the cascode devices. Run OP simulation. Find the percent change in I_{out} .

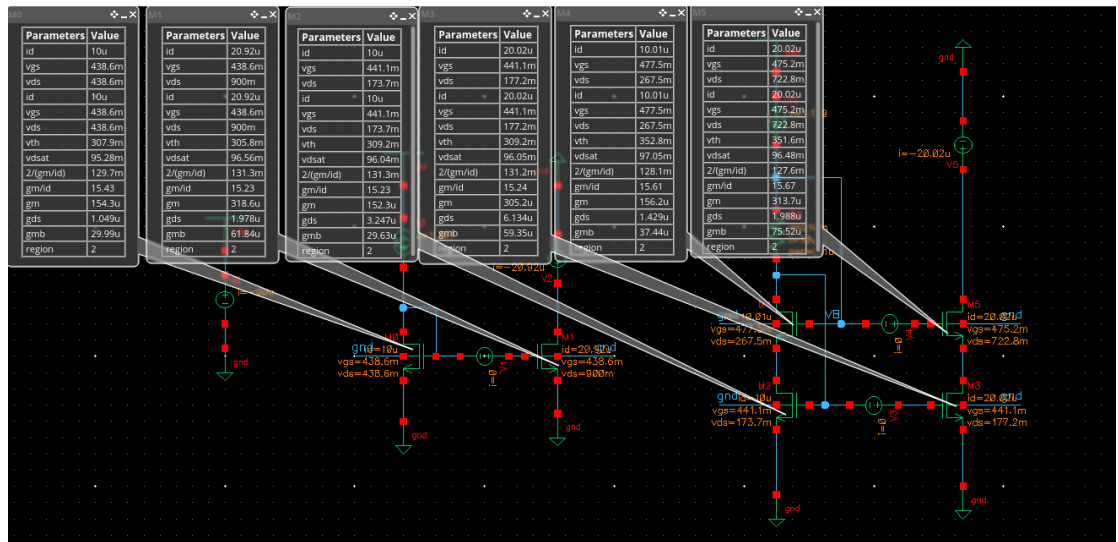


Figure 14 schematic with mismatch in V_{TH}

For simple CS : the percent change in $I_{out} = \frac{20.9u - 20.9u}{20.9u} = 0$

For Cascoded CS : the percent change in $I_{out} = \frac{20u - 21.3u}{20u} = 0$

4) Analytically calculate the percent change in I_{out} and compare it to the simulation result.

$$\frac{\Delta I}{I} = G_M \Delta V = \frac{g_{m5} g_{ds3}}{((g_{m5} + g_{mb5})) I_D} * V_{MIS2} * 100 = \frac{313.7 * 6.13}{((313.7 + 75.5)) * 20} * V_{MIS2} * 100 = 0.031\%$$

	Simulator	Analytical
Error%	0%	0.031%

5) Which mismatch contribution is more pronounced? Why?

V_{MIS1} in the (M0,M1) and (M2,M3) is more pronounced as it effect on the V_{gs} transistors that has direct effect on the current, but the mismatch V_{MIS2} in (M4,M5) effect on V_{ds} of the mirror that has weak effect on the current.

6) Which design decision is better: setting the same W and L for the mirror and cascode devices? Or using larger W and L for the current mirror devices? Why?

Using larger W and L for the current mirror devices is better, as increasing the area decrease the effect of the mismatch, we can't make it very large as the area of chip is proportional to the cost.