

# Analog IC Design – Cadence Tools

Lab 03

Cascode Amplifier

## PART 2: Cascode for Gain

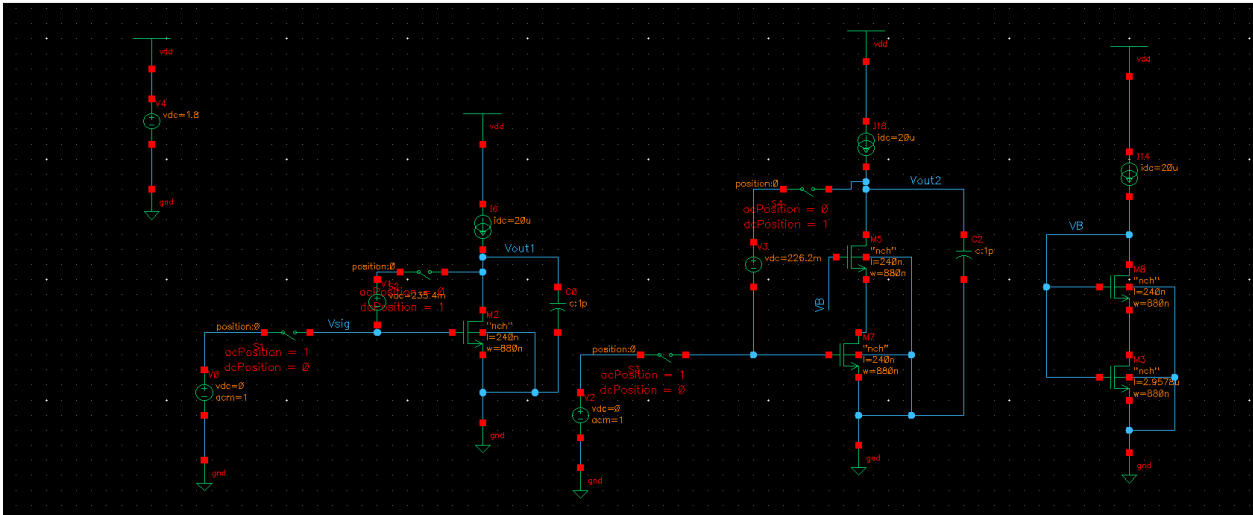


Figure 1 schematic

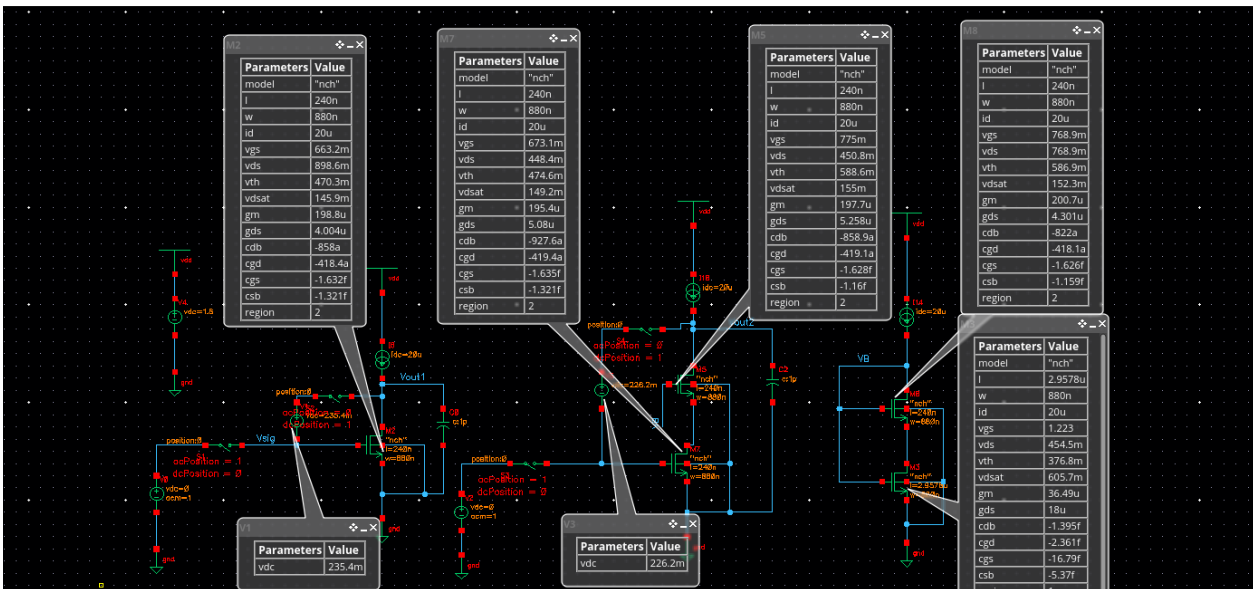


Figure 2 balloons

	M2	M3	M5	M7	M8
Gmb	48.32u	10.47u	42.14u	47.62u	42.63u

Transistors M[2,5,7] are in saturations (region = 2)

Transistor M3 is in triode (region 1), because its  $V_{gs} = V_B$ , and its  $V_{ds} = V_B - V_{ds}(M0)$

$\therefore V_{gs} > V_{ds}$ ,  $\therefore$  Transistor M3 is in triode.

### Vth for M2 & M7 & M5

$V_{TH}$  for M2 & M7 are the same, but M5 is different, because of the source body effect.

$$V_{TH} = V_{TH0} + \gamma(\sqrt{2\phi_F + V_{SB}} - \sqrt{2\phi_F})$$

Transistors have the different  $V_{th}$ , because  $V_{th}$  depend on the value of  $V_{SB}$  and as  $V_B$  is grounded, so the value of  $V_{th}$  will depend only on  $V_S$ , so as shown  $V_{th1}$  and  $V_{th2}$  are equal because  $V_S$  is equal and  $V_{th3}$  is different from them because its value of  $V_S$  is different.

( Note that M[2,5,7] transistors are identical, but M[3] isn't, as it has different L)

7)  $g_m \gg g_{ds}$

8)  $g_m > g_{mb}$

9)  $c_{gs} > c_{gd}$

10)  $c_{sb} > c_{db}$

## 2. AC Analysis

Name	Type	Details	Value	Plot
	expr	$V_F/V_{out1}$		<input checked="" type="checkbox"/>
	expr	$dB20(V_F/V_{out1})$		<input checked="" type="checkbox"/>
	expr	$ymax(dB20(V_F/V_{out1}))$	33.92	<input checked="" type="checkbox"/>
	expr	$ymax(mag(V_F/V_{out1}))$	49.65	<input checked="" type="checkbox"/>
	expr	$bandwidth(V_F/V_{out1})$ 3 "low"	635.2K	<input checked="" type="checkbox"/>
	expr	$gainBwProd(V_F/V_{out1})$	31.62M	<input checked="" type="checkbox"/>
	expr	$V_F/V_{out2}$		<input checked="" type="checkbox"/>
	expr	$dB20(V_F/V_{out2})$		<input checked="" type="checkbox"/>
	expr	$ymax(dB20(V_F/V_{out2}))$	65.07	<input checked="" type="checkbox"/>
	expr	$ymax(mag(V_F/V_{out2}))$	1.792K	<input checked="" type="checkbox"/>
	expr	$bandwidth(V_F/V_{out2})$ 3 "low"	16.98K	<input checked="" type="checkbox"/>
	expr	$gainBwProd(V_F/V_{out2})$	30.52M	<input checked="" type="checkbox"/>

Figure 3 circuit parameters

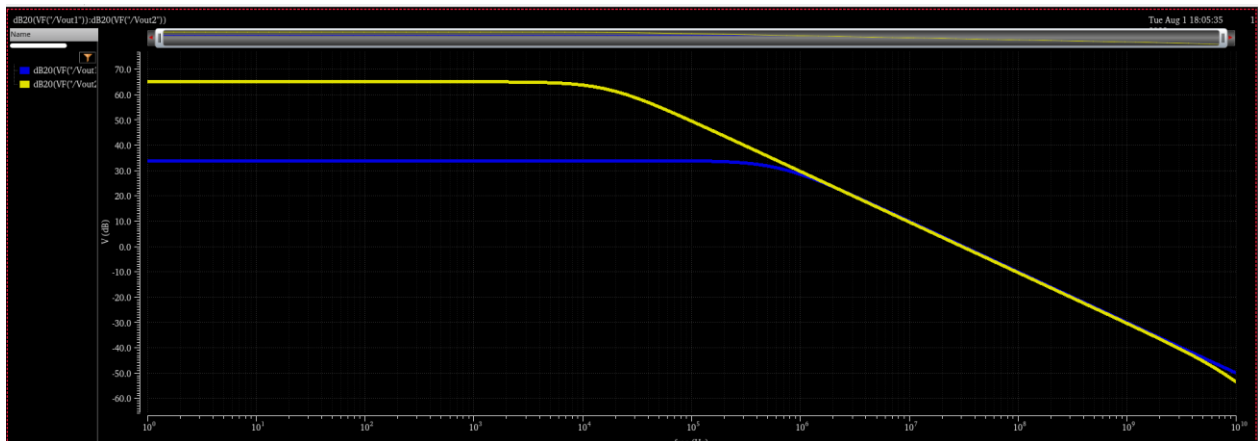


Figure 4 Bode plot (magnitude) of CS and cascode

### Hand analysis:

$C_{out} = 1p$ , as all parasitic capacitances  $\ll 1p$ , and in parallel with it.

$$r_o = \frac{1}{g_{ds}}$$

$$DC\ gain\ (CS) = -g_m * r_o = \frac{-g_{m2}}{g_{ds2}} = \frac{-198.8}{4} = -49.7$$

$$r_{o5t} = (r_{o7} + r_{o5} + (g_{m5} + g_{mb5}) * r_{o5} * r_{o7})$$

$$r_{o5t} = \left( \frac{1}{5.258\mu} + \frac{1}{5.08\mu} + (197.7\mu + 42.14\mu) * \frac{1}{5.258\mu} * \frac{1}{5.08\mu} \right) = 9.366M$$

$$DC\ gain\ (Cascode) = -g_{m7} * r_{o5t} = -195.4u * 9.366M = -1830 = -1.83K$$

$$BW(CS) = \frac{1}{2 * \pi * r_o * C} = \frac{4u}{2 * \pi * 1p} = 636.62K$$

$$BW(Cascode) = \frac{1}{2 * \pi * r_{o5t} * C} = \frac{1}{2 * \pi * 9.366M * 1p} = 17K$$

$$GBW(CS) = BW1 * DC\ gain\ 1 = 31.64M$$

$$GBW(Cascode) = BW2 * DC\ gain\ 2 = 31.11M$$

*GPW analytically is UGF (unity gain frequency)*

	Simulation	Hand analysis
DC Gain (CS)	49.65	49.7
$BW(CS)$	635.2K	636.62K
$GBW(CS)$	31.62M	31.64M
DC Gain (Cascode)	17.92K	1.83K
$BW(Cascode)$	16.98K	17K
$GBW(Cascode)$	30.52M	31.11M

#### Comments:

The Cascode amplifier Gain is higher than the common-source amplifier Gain, as The Cascode amplifier has higher Rout and  $DC\ gain = -g_m * r_o$ .

The Cascode amplifier Bandwidth is lower than the common-source amplifier Bandwidth, as The Cascode amplifier has higher Rout and  $BW = \frac{1}{2 * \pi * r_o * C}$ .

I didn't use the parasitic capacitances as  $1p \gg$  from it

PART 3 [Optional]: Cascode for BW

1. OP Analysis

$RD = 0.9/20u = 45K$

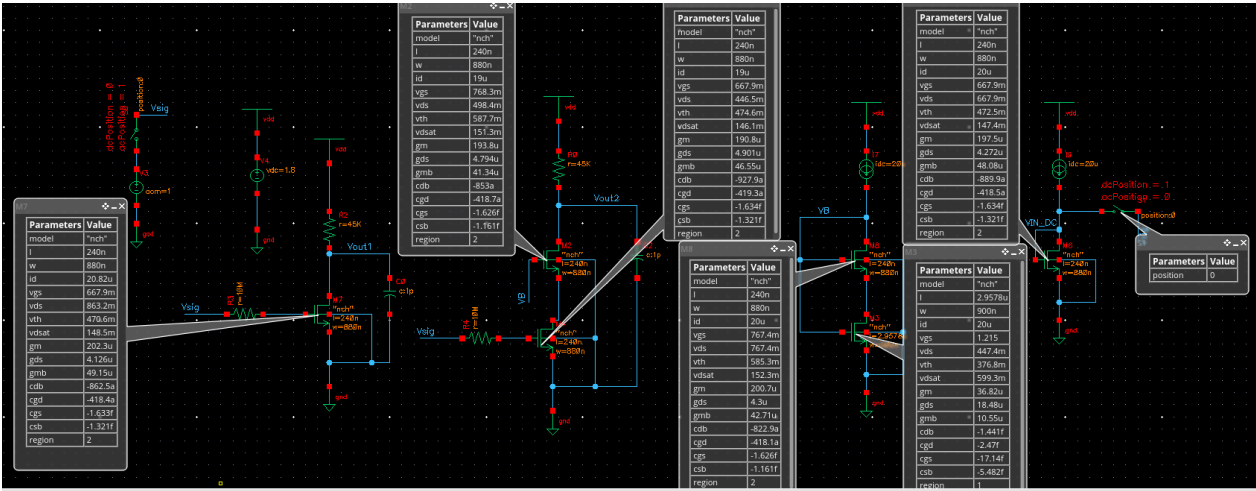


Figure 5 balloons of CS and cascode

4) All transistor (CM & Cascode) have (region = 2), that is mean that all of them is in saturation region.

2. AC Analysis

Name	Type	Details	Value	Plot	Save	Spec
	expr	VR"/Vout1")		<input checked="" type="checkbox"/>	<input type="checkbox"/>	
	expr	dB20(VR"/Vout1")		<input checked="" type="checkbox"/>	<input type="checkbox"/>	
	expr	ymax(dB20(VR"/Vout1"))	17.71	<input checked="" type="checkbox"/>	<input type="checkbox"/>	
	expr	ymax(mag(VR"/Vout1"))	7.678	<input checked="" type="checkbox"/>	<input type="checkbox"/>	
	expr	bandwidth(VR"/Vout1") 3 "low"	2.962M	<input checked="" type="checkbox"/>	<input type="checkbox"/>	
	expr	gainBwProd(VR"/Vout1")	22.79M	<input checked="" type="checkbox"/>	<input type="checkbox"/>	
	expr	VR"/Vout2")		<input checked="" type="checkbox"/>	<input type="checkbox"/>	
	expr	dB20(VR"/Vout2")		<input checked="" type="checkbox"/>	<input type="checkbox"/>	
	expr	ymax(dB20(VR"/Vout2"))	18.46	<input checked="" type="checkbox"/>	<input type="checkbox"/>	
	expr	ymax(mag(VR"/Vout2"))	8.378	<input checked="" type="checkbox"/>	<input type="checkbox"/>	
	expr	bandwidth(VR"/Vout2") 3 "low"	6.224M	<input checked="" type="checkbox"/>	<input type="checkbox"/>	
	expr	gainBwProd(VR"/Vout2")	52.27M	<input checked="" type="checkbox"/>	<input type="checkbox"/>	

Figure 6 circuit parameters

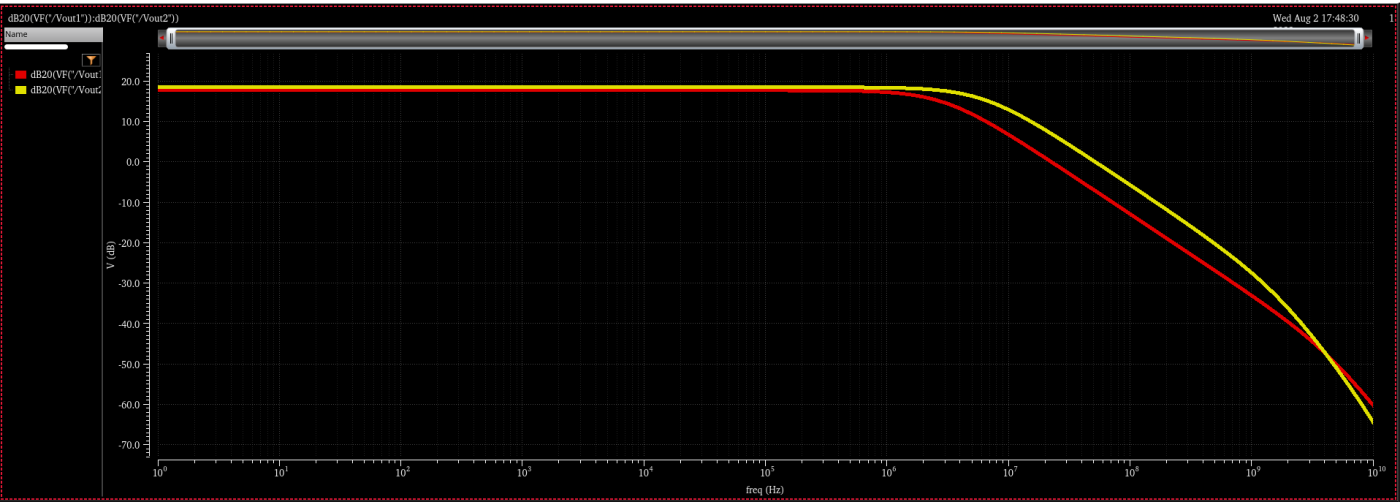


Figure 7 Bode plot (magnitude) of CS and cascode

## Hand analysis:

C (out) =1P, as all parasitic capacitances << 1P , and in parallel with it.

$$r_o = \frac{1}{g_{ds}}$$

$$r_{ot(CS)} = \frac{1}{g_{ds7}} || R_D = \frac{1}{4.126\mu} || 45K = 37.95K$$

$$DC\ gain\ (CS) = -g_m * r_o = -202.3\mu * 37.95K = -7.677$$

$$r_{ot(Cascode)} = (r_{o4} + r_{o5} + (g_{m5} + g_{mb5}) * r_{o5} * r_{o4}) || R_D$$

$$r_{ot(Cascode)} = \left( \frac{1}{4.9\mu} + \frac{1}{4.8\mu} + (193.8\mu + 41.34\mu) * \frac{1}{4.9\mu} * \frac{1}{4.8\mu} \right) || R_D = 10.4M || 45K = 44.8K$$

$$DC\ gain\ (Cascode) = -g_{m4} * r_{ot(Cascode)} = -190.8\mu * 44.8K = -8.548$$

R dominant is 10M at the input

$$BW(CS) = \frac{1}{2*\pi*r_o*C} = \frac{1}{2\pi*10^7*((1+7.677)*418.4a+1.633f)} = 2.6M$$

$$BW(Cascode) = \frac{1}{2*\pi*r_{ot}*C} = \frac{1}{2\pi*10^7*((1+1.1935)*418.1a+1.634f)} = 6.2M$$

$$GBW(CS) = BW1 * DC\ gain\ 1 = 20\ M$$

$$GBW(Cascode) = BW2 * DC\ gain\ 2 = 53M$$

GPW analytically is UGF (unity gain frequency)

	Simulation	Hand analysis
DC Gain (CS)	7.678	7.677
$BW(CS)$	2.962M	2.6M
$GBW(CS)$	22.79M	20M
DC Gain (Cascode)	8.378	8.548
$BW(Cascode)$	6.224M	6.2M
$GBW(Cascode)$	52.27M	53M

## Comments:

The Cascode amplifier Gain is higher than the common-source amplifier Gain, as The Cascode amplifier has higher Rout and  $DC\ gain = -g_m * r_o$ .

The Cascode amplifier Bandwidth is lower than the common-source amplifier Bandwidth, as The Cascode amplifier has higher Rout and  $BW = \frac{1}{2*\pi*r_o*C}$ .

The Gain in this case is lower than the gain in part 2 because we used Resistance instead of the ideal current source which made the output resistance lower.